



香港中文大學(深圳)  
The Chinese University of Hong Kong, Shenzhen

Last update: 2023/2/9

# EIE 2050 Digital Logic and Systems

## Chapter 4 : Boolean Algebra and Logic Simplification

Simon Pun, Ph.D.



香港中文大學(深圳)  
The Chinese University of Hong Kong, Shenzhen

# Last Week

## ❑ Logic gates

- ◆ Inverter, AND, OR, NAND, NOR, XOR, XNOR
- ◆ Truth Tables, Distinctive Shape Symbols

## ❑ Performance Characteristics and Parameters

- ◆ Propagation Delay Time
- ◆ DC Supply Voltage
- ◆ Power Dissipation
- ◆ Input and Output Logic Levels
- ◆ Speed-Power Product (SPP)
- ◆ Fan-Out and Loading

## ❑ Troubleshooting

- ◆ Internal Failures of IC Logic Gates
- ◆ External Opens and Shorts



# Boolean Operations and Expressions

- ❑ Boolean Addition : Equivalent to the OR operation

## EXAMPLE 4-1

Determine the values of A, B, C, and D that make the sum term  $A + \bar{B} + C + \bar{D}$  equal to 0.

Solution :

$$A = 0, \bar{B} = 0, C = 0, \bar{D} = 0 \quad \longrightarrow \quad A = 0, B = 1, C = 0, D = 1$$

- ❑ Boolean Multiplication : Equivalent to the AND operation

## EXAMPLE 4-2

Determine the values of A, B, C, and D that make the product term  $A\bar{B}C\bar{D}$  equal to 1.

Solution :

$$A = 1, \bar{B} = 1, C = 1, \bar{D} = 1 \quad \longrightarrow \quad A = 1, B = 0, C = 1, D = 0$$



# Laws and Rules of Boolean Algebra

## □ Laws of Boolean Algebra

- ◆ Commutative laws  $A + B = B + A$   $AB = BA$
- ◆ Associative laws  $A + (B + C) = (A + B) + C$   $A(BC) = (AB)C$
- ◆ Distributive law  $A(B + C) = AB + AC$

## □ Rules of Boolean Algebra

**TABLE 4-1**

Basic rules of Boolean algebra.

- |                      |                               |
|----------------------|-------------------------------|
| 1. $A + 0 = A$       | 7. $A \cdot A = A$            |
| 2. $A + 1 = 1$       | 8. $A \cdot \bar{A} = 0$      |
| 3. $A \cdot 0 = 0$   | 9. $\bar{\bar{A}} = A$        |
| 4. $A \cdot 1 = A$   | 10. $A + AB = A$              |
| 5. $A + A = A$       | 11. $A + \bar{A}B = A + B$    |
| 6. $A + \bar{A} = 1$ | 12. $(A + B)(A + C) = A + BC$ |

$A$ ,  $B$ , or  $C$  can represent a single variable or a combination of variables.



# Proof of Rule 10


**Rule 10:  $A + AB = A$**  This rule can be proved by applying the distributive law, rule 2, and rule 4 as follows:


$$\begin{aligned}
 A + AB &= A \cdot 1 + AB = A(1 + B) && \text{Factoring (distributive law)} \\
 &= A \cdot 1 && \text{Rule 2: } (1 + B) = 1 \\
 &= A && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

**TABLE 4-2**

Rule 10:  $A + AB = A$ . Open file T04-02 to verify.

$A$	$B$	$AB$	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

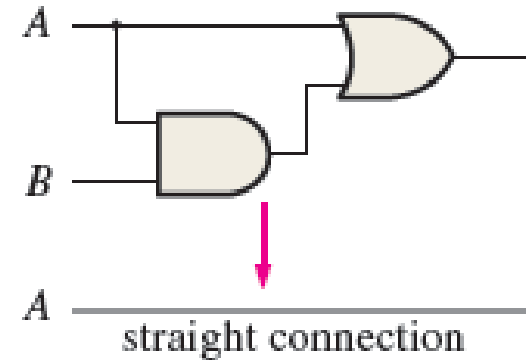

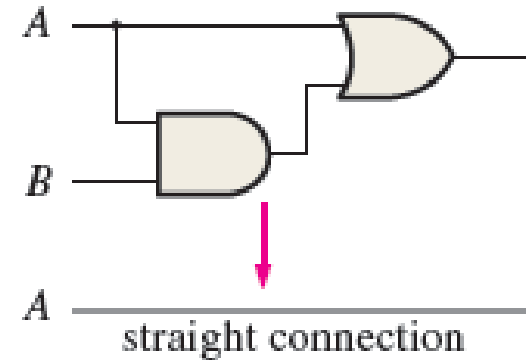

equal



# Proof of Rule 11

**Rule 11:  $A + \bar{A}B = A + B$**  This rule can be proved as follows:

$$A + \bar{A}B = (A + AB) + \bar{A}B$$

Rule 10:  $A = A + AB$

$$= (AA + AB) + \bar{A}B$$

Rule 7:  $A = AA$

$$= AA + AB + A\bar{A} + \bar{A}B$$

Rule 8: adding  $A\bar{A} = 0$

$$= (A + \bar{A})(A + B)$$


Factoring

$$= 1 \cdot (A + B)$$

Rule 6:  $A + \bar{A} = 1$

$$= A + B$$

Rule 4: drop the 1

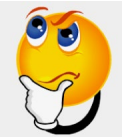


*Any better ways?*

**TABLE 4-3**

Rule 11:  $A + \bar{A}B = A + B$ . Open file T04-03 to verify.

A	B	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

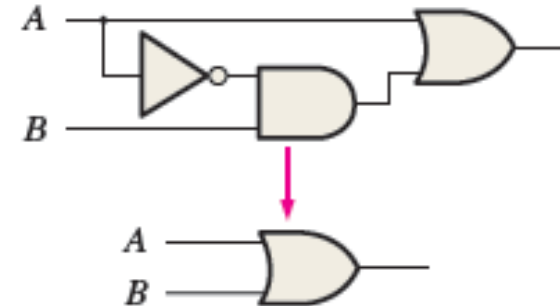

# Proof of Rule 12

**Rule 12:**  $(A + B)(A + C) = A + BC$  This rule can be proved as follows:

$$\begin{aligned}
 (A + B)(A + C) &= AA + AC + AB + BC && \text{Distributive law} \\
 &= A + AC + AB + BC && \text{Rule 7: } AA = A \\
 &= A(1 + C) + AB + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + AB + BC && \text{Rule 2: } 1 + C = 1 \\
 &= A(1 + B) + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + BC && \text{Rule 2: } 1 + B = 1 \\
 &= A + BC && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

**TABLE 4-4**

Rule 12:  $(A + B)(A + C) = A + BC$ . Open file T04-04 to verify.


A	B	C	A + B	A + C	(A + B)(A + C)	BC	A + BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑




# DeMorgan's Theorems

$$\overline{XY} = \bar{X} + \bar{Y}$$

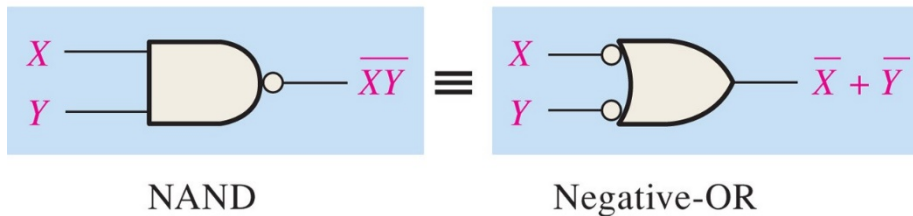

Inputs		Output	
X	Y	$\overline{XY}$	$\bar{X} + \bar{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

$$\overline{X + Y} = \bar{X}\bar{Y}$$

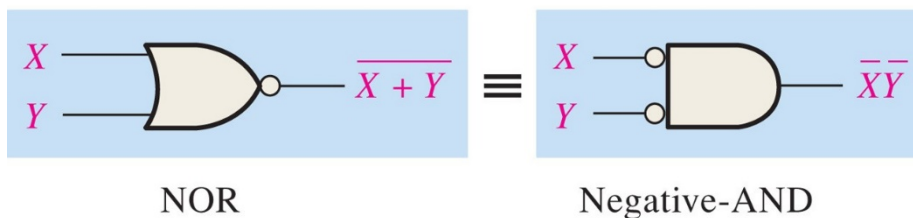

Inputs		Output	
X	Y	$\overline{X + Y}$	$\bar{X}\bar{Y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0





# DeMorgan's Theorems : Examples

## Example 4-6

Apply DeMorgan's theorems to each expression:

(a)  $\overline{\overline{(A + B)} + \overline{C}}$

(b)  $\overline{(\overline{A} + B) + CD}$

(c)  $\overline{(A + B)\overline{C}\overline{D} + E + \overline{F}}$

Basic rules of Boolean algebra.

1.  $A + 0 = A$

2.  $A + 1 = 1$

3.  $A \cdot 0 = 0$

4.  $A \cdot 1 = A$

5.  $A + A = A$

6.  $A + \overline{A} = 1$

7.  $A \cdot A = A$

8.  $A \cdot \overline{A} = 0$

9.  $\overline{\overline{A}} = A$

10.  $A + \overline{A}B = A$

11.  $A + \overline{A}B = A + B$

12.  $(A + B)(A + C) = A + BC$

## Solution

(a)  $\overline{\overline{(A + B)} + \overline{C}} = \overline{\overline{(A + B)}}\overline{\overline{C}} = (A + B)C$


(b)  $\overline{(\overline{A} + B) + CD} = \overline{(\overline{A} + B)}\overline{CD} = (\overline{\overline{A}}\overline{B})(\overline{C} + \overline{D}) = A\overline{B}(\overline{C} + \overline{D})$

(c)  $\overline{(A + B)\overline{C}\overline{D} + E + \overline{F}} = \overline{((A + B)\overline{C}\overline{D})(E + \overline{F})} = (\overline{A}\overline{B} + C + D)\overline{E}\overline{F}$


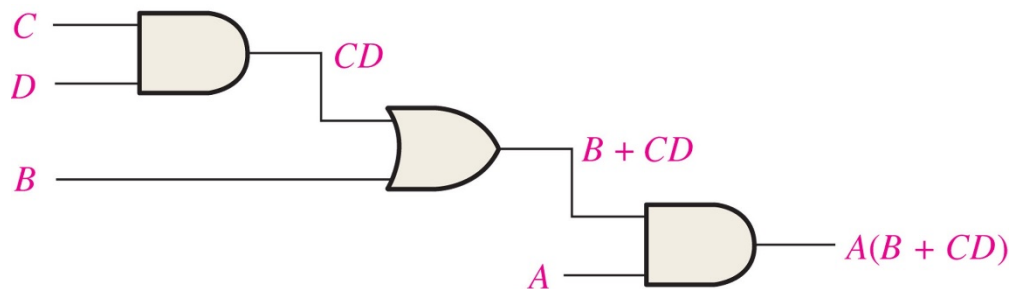
# Boolean Analysis of Logic Circuits

- ❑ First, derive the Boolean expression for a given combinational logic circuit;



- ❑ Then, construct the truth table.

**TABLE 4-5**

Truth table for the logic circuit in Figure 4-18.

Inputs				Output
$A$	$B$	$C$	$D$	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1



# Logic Simplification Using Boolean Algebra

- Use the basic laws, rules, and theorems of Boolean algebra to manipulate and simplify an expression.

**Example 4-7** Using Boolean algebra techniques, simplify this expression:

$$\begin{aligned} & AB + A(B + C) + B(B + C) \\ &= \underbrace{AB + AB}_{\text{Rule 5}} + AC + \underbrace{BB}_{\text{Rule 7}} + BC \quad \text{distributive law} \\ &= AB + AC + \underbrace{B + BC}_{\text{Rule 10}} \\ &= \underbrace{AB}_{\text{Rule 10}} + AC + \underbrace{B}_{\text{Rule 10}} \\ &= AC + B \end{aligned}$$

1.  $A + 0 = A$

2.  $A + 1 = 1$

3.  $A \cdot 0 = 0$

4.  $A \cdot 1 = A$

5.  $A + A = A$

6.  $A + \bar{A} = 1$

7.  $A \cdot A = A$

8.  $A \cdot \bar{A} = 0$

9.  $\bar{\bar{A}} = A$

10.  $A + AB = A$

11.  $A + \bar{A}B = A + B$

12.  $(A + B)(A + C) = A + BC$



# Standard Forms of Boolean Expressions

## □ The Sum-of-Products (SOP) Form

$$(A\bar{B} + \bar{C}) = (A + \bar{C})(\bar{B} + \bar{C})$$


- ◆ **Domain** : the set of variables contained in the expression in either complemented or uncomplemented form.
- ◆ SOP form: 2+ product terms are summed by Boolean addition
- ◆ Overbar:  $\overline{ABC}$  ✓  $\overline{A}BC$  ✗
- ◆ Conversion to SOP form:  $A(B+CD) = AB+ACD$
- ◆ The **standard** SOP form : all the variables in the domain appear in each product term in the expression.

$$A\bar{B}C + ABC\bar{D} = A\bar{B}C(D + \bar{D}) + ABC\bar{D} = A\bar{B}CD + A\bar{B}C\bar{D} + ABC\bar{D}$$

## □ The Product-of-Sums (POS) Form

- ◆ POS form: 2+ sum terms are multiplied

$$(A\bar{B} + \bar{C})(A + B)$$

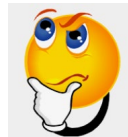

POS?

- ◆ The **standard** POS form:

**Domain** : A, B, C, D

$$\begin{aligned} A + \bar{B} + C &= A + \bar{B} + C + D\bar{D} \\ &= (A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D}) \end{aligned}$$



# The Standard POS Form

Recall Rule # 12.  $(A + B)(A + C) = A + \overline{B}C$

$$P = \underbrace{P + D\overline{D}}_{= (P + D)(P + \overline{D})} = \underbrace{P + PD + P\overline{D}}_{= (P + D)(P + \overline{D})} + D\overline{D}$$



Domain : A, B, C, D

$$\begin{aligned} A + \overline{B} + C &= A + \overline{B} + C + D\overline{D} \\ &= (A + \overline{B} + C + D)(A + \overline{B} + C + \overline{D}) \end{aligned}$$

Now, back to our example  $(A\overline{B} + \overline{C})(A + B)$

$$A\overline{B} + \overline{C} = (A + \overline{C})(\overline{B} + \overline{C}) = \boxed{(A + B + \overline{C})} \boxed{(A + \overline{B} + \overline{C})} \boxed{(A + \overline{B} + \overline{C})} (\overline{A} + \overline{B} + \overline{C})$$

$$A + B = \boxed{(A + B + C)} \boxed{(A + B + \overline{C})}$$

$$\Rightarrow (A\overline{B} + \overline{C})(A + B) = (A + B + C)(A + B + \overline{C})(A + \overline{B} + \overline{C})(\overline{A} + \overline{B} + \overline{C})$$



# Boolean Expressions and Truth Tables (I)

## Example 4-20

Develop a truth table for the standard SOP expression :  $\bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$

A	B	C	$\bar{A}\bar{B}C$	$A\bar{B}\bar{C}$	$ABC$	Output
0	0	0				0
0	0	1	1	Don't Care		1
0	1	0				0
0	1	1				0
1	0	0	Don't Care	1	Don't Care	1
1	0	1				0
1	1	0				0
1	1	1	Don't Care		1	1



# Boolean Expressions and Truth Tables (II)

**Example 4-21** Determine the truth table for the following standard POS expression:

$$(A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

A	B	C	$(A + B + C)$	$(A + \bar{B} + C)$	$(A + \bar{B} + \bar{C})$	$(\bar{A} + B + \bar{C})$	$(\bar{A} + \bar{B} + C)$	Output
0	0	0	0	Don't Care				0
0	0	1						1
0	1	0	Don't Care	0	Don't Care			0
0	1	1			0			0
1	0	0						1
1	0	1	Don't Care			0	Don't Care	0
1	1	0	Don't Care				0	0
1	1	1						1



# From Truth Tables to Standard Expressions

**Example 4-22** Determine the truth table for the following standard SOP expression:

**TABLE 4-8**

Inputs			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\Rightarrow \bar{A}BC$   
 $\Rightarrow A\bar{B}\bar{C}$   
 $\Rightarrow AB\bar{C}$   
 $\Rightarrow ABC$

$X = \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C} + ABC$





# From Truth Tables to Standard Expressions


**Example 4-22** Determine the truth table for the following standard POS expression:

**TABLE 4-8**

Inputs			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\Rightarrow A + B + C$   
 $\Rightarrow A + B + \bar{C}$   
 $\Rightarrow A + \bar{B} + C$   
 $\Rightarrow \bar{A} + B + \bar{C}$

}

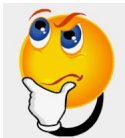

*Any more solutions?*



$$X = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + \bar{C})$$



# The Karnaugh Map (K-Map)

- ❑ A **systematic** method to simplify Boolean expressions to their simplest SOP/POS expressions, aka. the minimum expressions
- ❑ Cells : each represents a binary value of the input variables
  - ◆ # of **cells** : the total # of possible input variable combinations
  - ◆ Adjacent cells are indexed with the **Gray code**, i.e. only a single variable change between adjacent

A 3-variable K-map


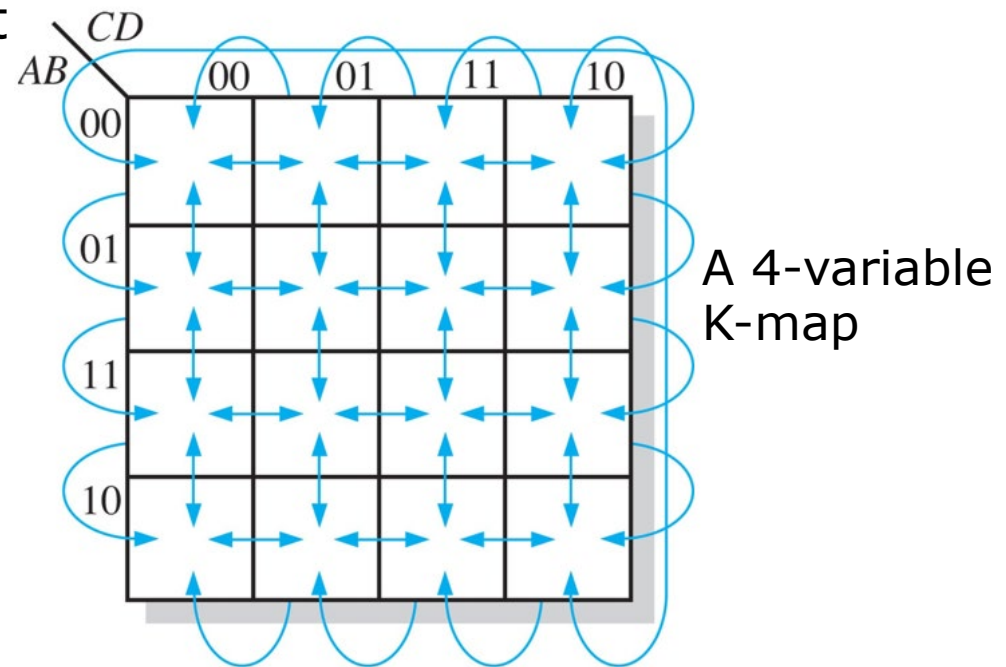
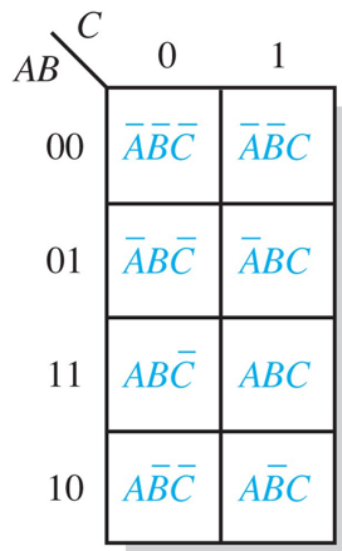


# Karnaugh Map SOP Minimization (I)

Example 4-27

$$\bar{A}\bar{B}\bar{C} + \overbrace{\bar{A}BC}^{BC} + \underbrace{ABC + AB\bar{C}}_{AB} = \bar{A}\bar{B}\bar{C} + \bar{A}BC + \boxed{ABC + AB\bar{C}} + AB\bar{C}$$

$$= \bar{A}\bar{B}\bar{C} + BC + AB$$

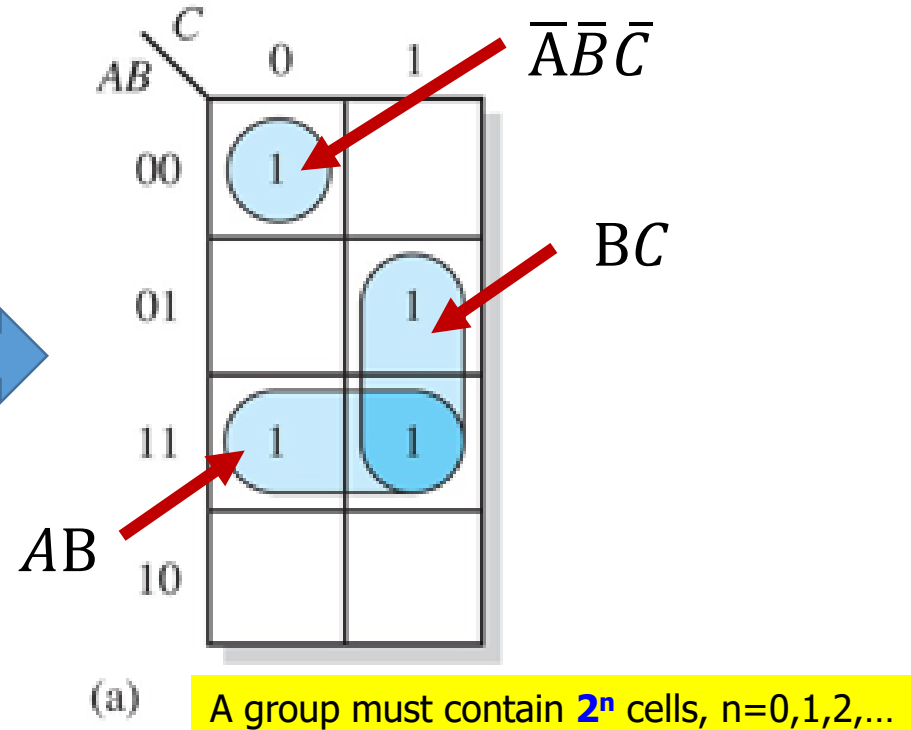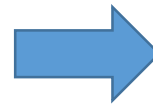
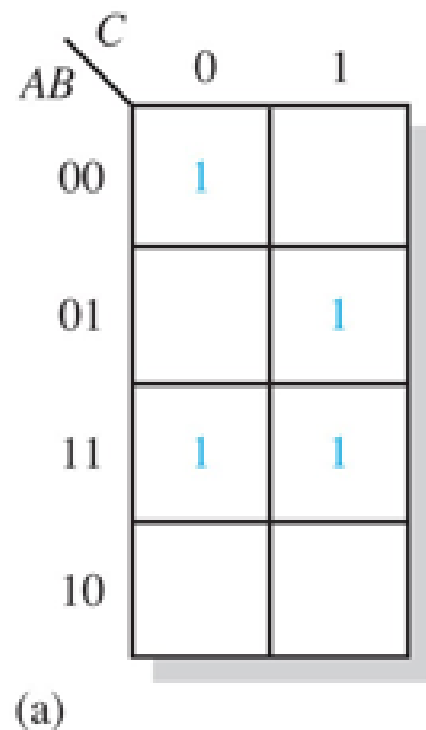


# Karnaugh Map SOP Minimization (II)

**Example 4-27**  $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC + A\bar{B}\bar{C} + A\bar{B}C = \bar{A}\bar{C} + AC + \bar{B}$

AB \ C		
	0	1
00	1	1
01	1	
11		1
10	1	1

(b)

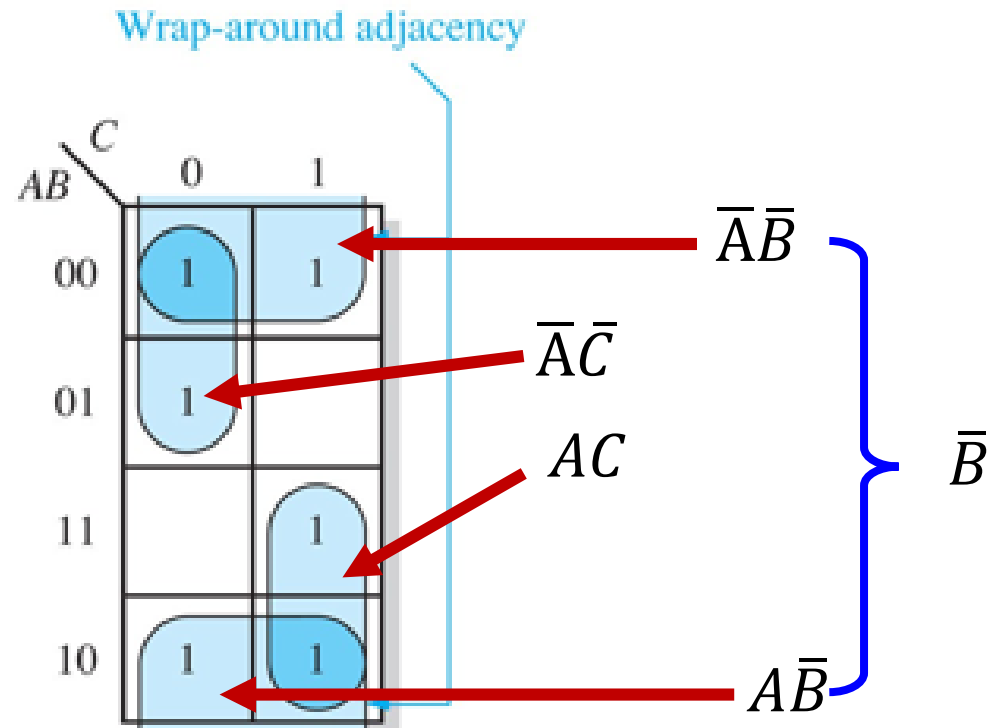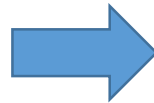


(b)




# Karnaugh Map SOP Minimization (III)

Example 4-27

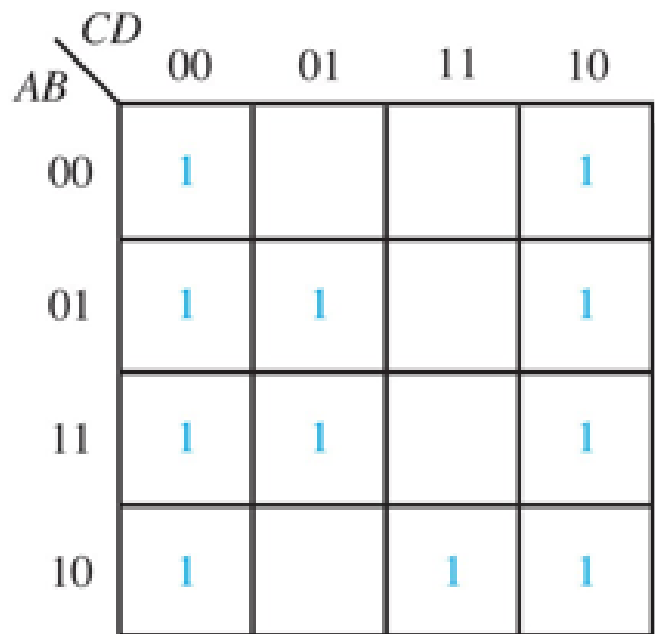

(d)

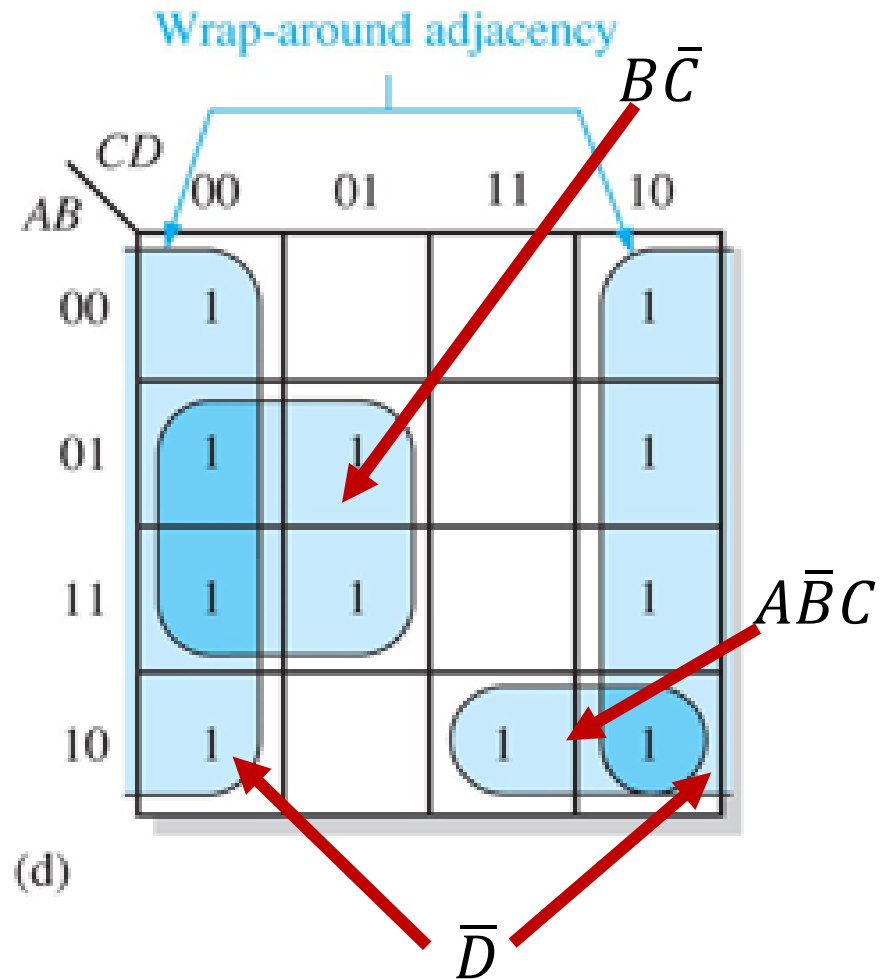


(d)



# Mapping Directly from a Truth Table

$$X = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + ABC$$

Inputs			Output
A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

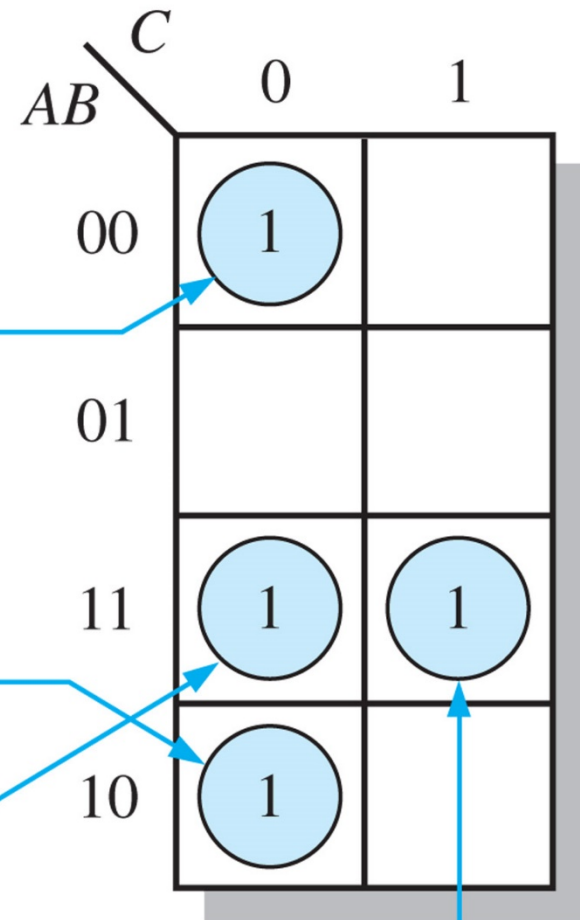


# “Don’t Care” Conditions

Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

(a) Truth table

- ❑ “don’t care” can be either a 1 or a 0
- ❑ When grouping the 1s, the “don’t care” terms (X’s) can be treated as 1s to make a larger grouping


Don’t cares

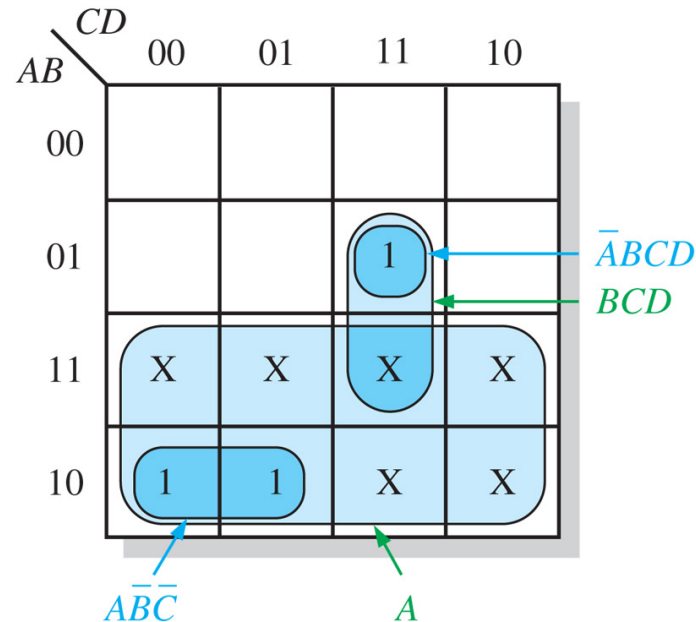

- (b) Without “don’t cares”  $Y = A\bar{B}\bar{C} + \bar{A}BCD$   
 With “don’t cares”  $Y = A + BCD$



# EXAMPLE 4–32 (I)

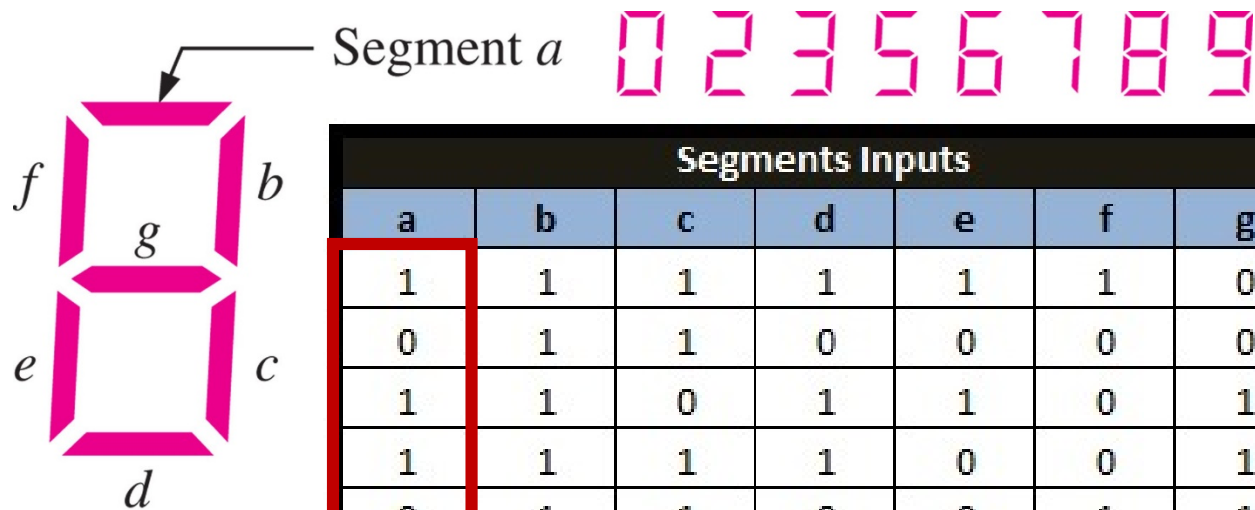

Segments Inputs							7 Segment Display Output				
a	b	c	d	e	f	g		A	B	C	D
1	1	1	1	1	1	0	0	0	0	0	0
0	1	1	0	0	0	0	1	0	0	0	1
1	1	0	1	1	0	1	2	0	0	1	0
1	1	1	1	0	0	1	3	0	0	1	1
0	1	1	0	0	1	1	4	0	1	0	0
1	0	1	1	0	1	1	5	0	1	0	1
1	0	1	1	1	1	1	6	0	1	1	0
1	1	1	0	0	0	0	7	0	1	1	1
1	1	1	1	1	1	1	8	1	0	0	0
1	1	1	1	0	0	1	9	1	0	0	1

**TABLE 2–5**

Each digit can be represented by a BCD code

Decimal/BCD conversion.

Decimal Digit	0	1	2	3	4	5	6	7	8	9
BCD	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001






# EXAMPLE 4-32 (II)

Truth table for Segment a

A	B	C	D	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X


AB \ CD	00	01	11	10
00	1		1	1
01		1	1	1
11	X	X	X	X
10	1	1	X	X
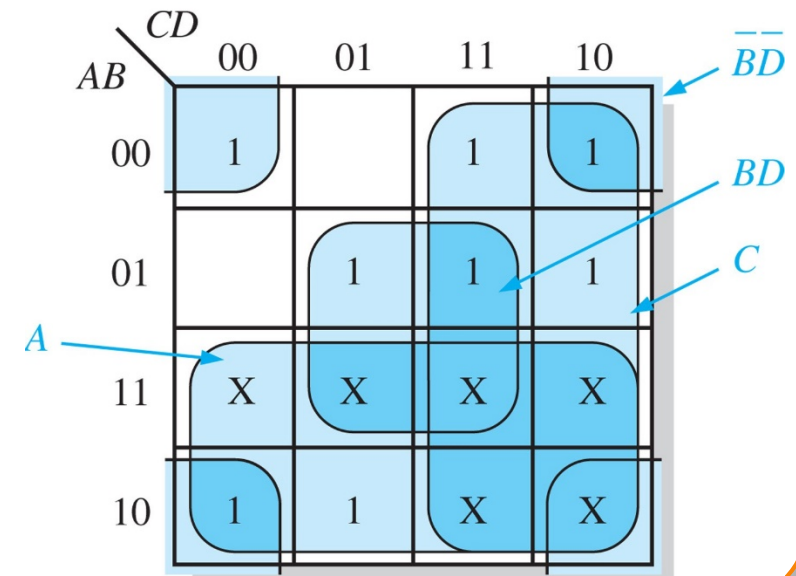
$$a = A + C + BD + \overline{B}\overline{D}$$



# Karnaugh Map POS Minimization (I)

- ❑ In SOP minimization, we focus on those 1's
- ❑ In **POS** minimization, we focus on those **0's**

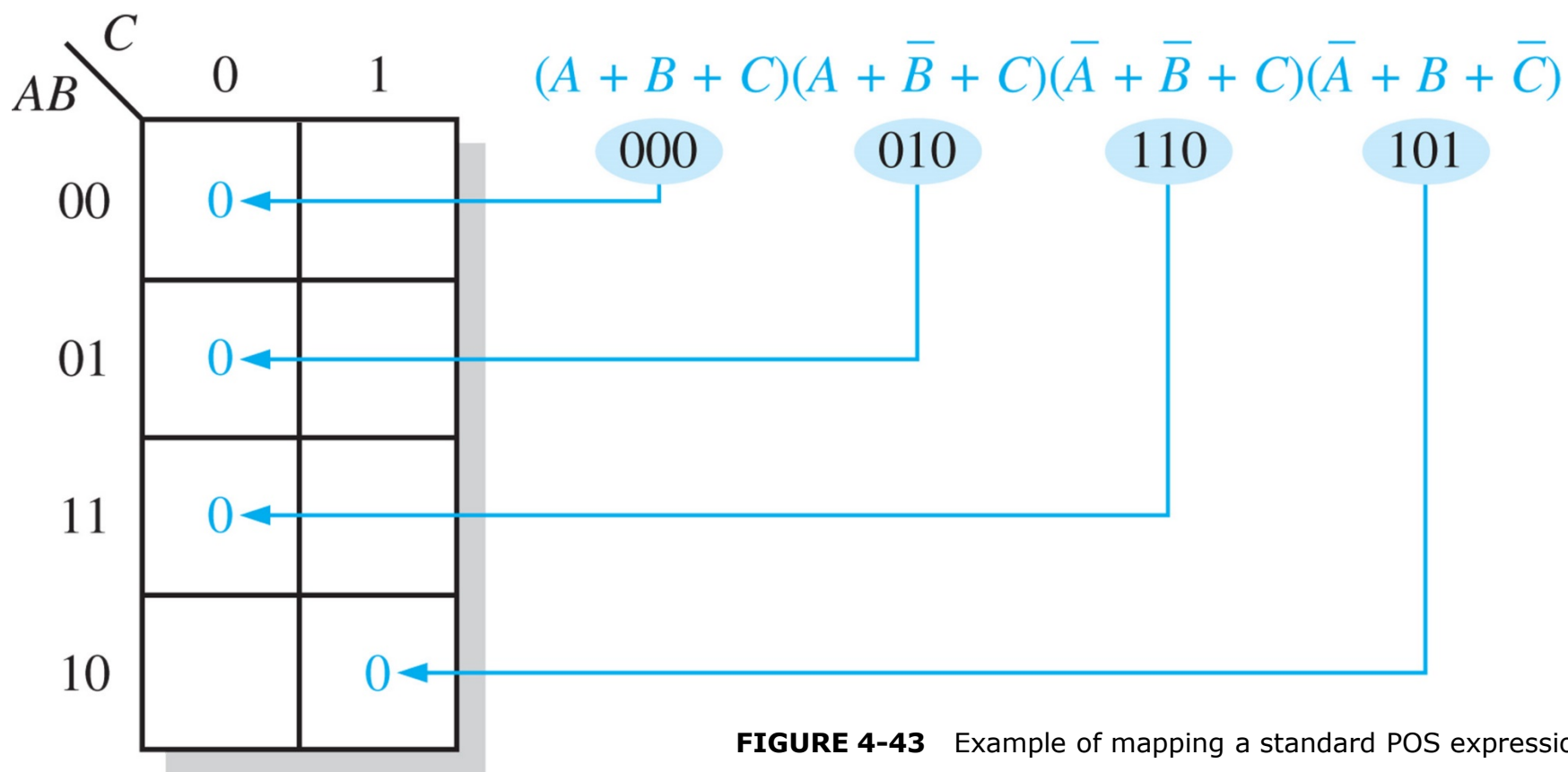

**FIGURE 4-43** Example of mapping a standard POS expression.




# Karnaugh Map POS Minimization (II)


**Example 4-34**  $(A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)$   
                     000                    001                    010                    011                    110

**Example 4-35**  $(B + C + D)(A + B + \bar{C} + D)(\bar{A} + B + C + \bar{D})(A + \bar{B} + C + D)(\bar{A} + \bar{B} + C + D)$   
                     X000                    0010                    1001                    0100                    1100

**Example 4-34**

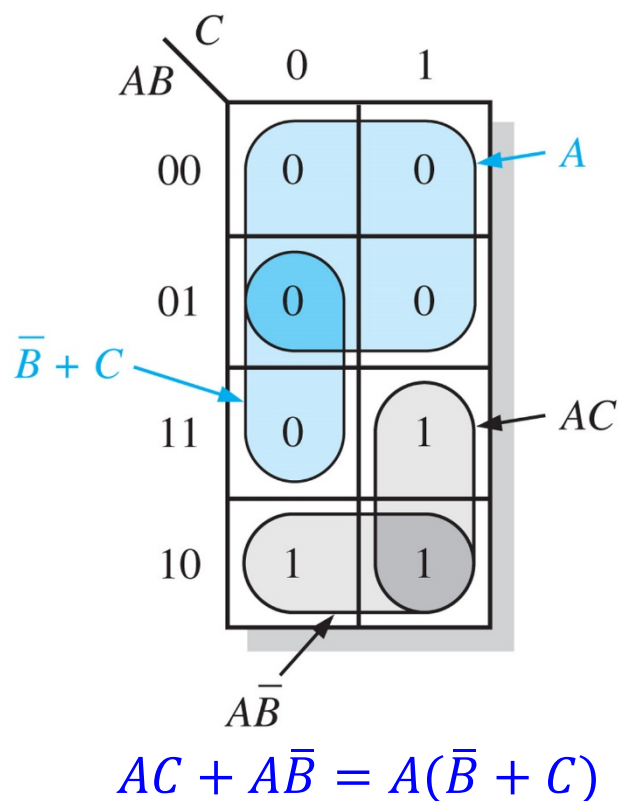

**Example 4-35**

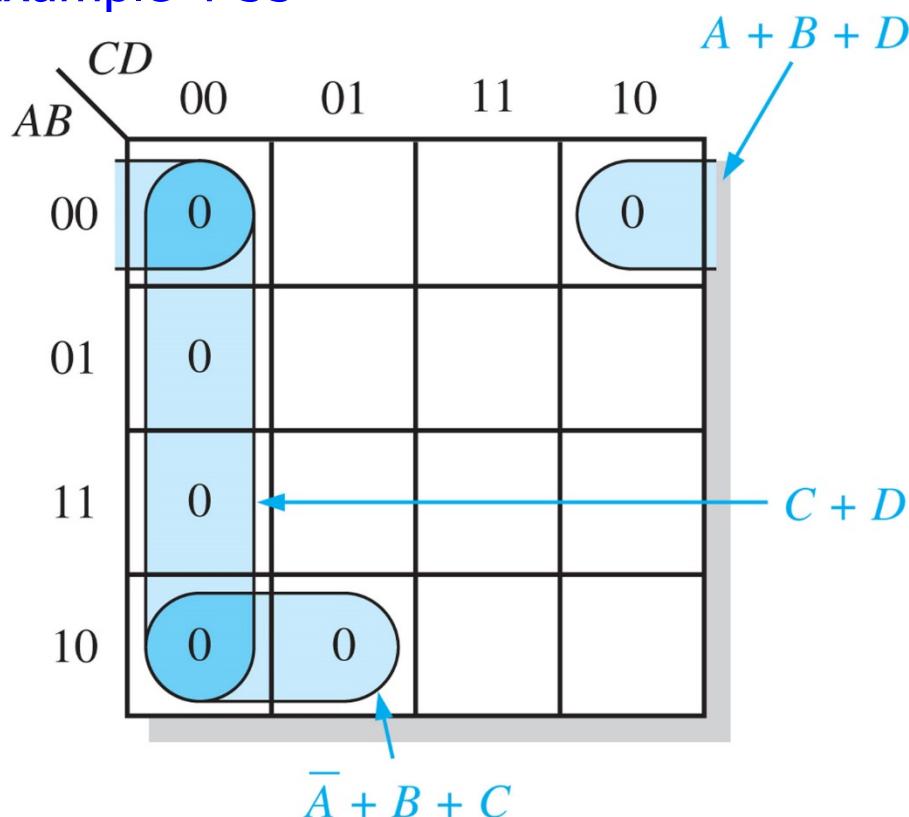

# Converting btw POS & SOP Using K-Map

**Example 4-35** Using a Karnaugh map, convert the following standard POS expression into a min. POS expression, a standard SOP expression, and a minimum SOP expression.

$$(\bar{A} + \bar{B} + C + D)(A + \bar{B} + C + D)(A + B + C + \bar{D})(A + B + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})(A + B + \bar{C} + D)$$

1

Find all 0's

1100

0100


0001

0011

1001


0010

2 Fill 0's

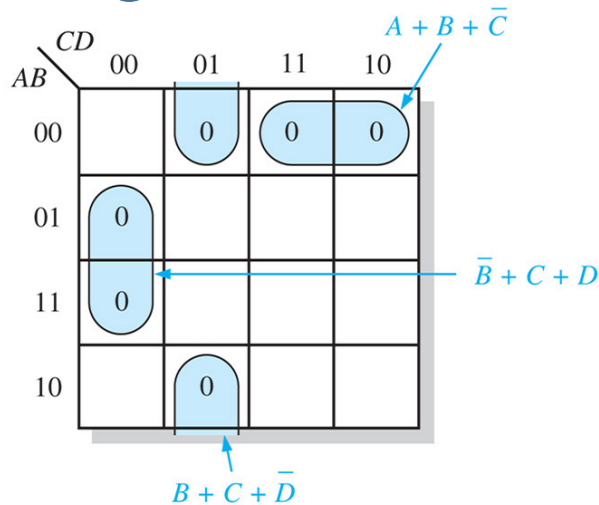

(a) Minimum POS:  $(A + B + C)(\bar{B} + \bar{C} + D)(B + C + \bar{D})$


3 Fill 1's

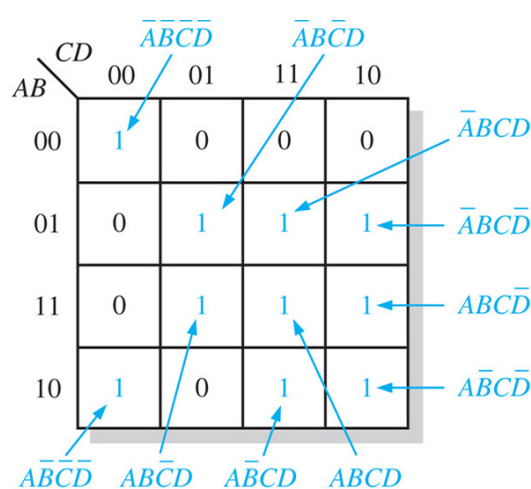

Standard SOP:

$$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D}$$

4 K-Map

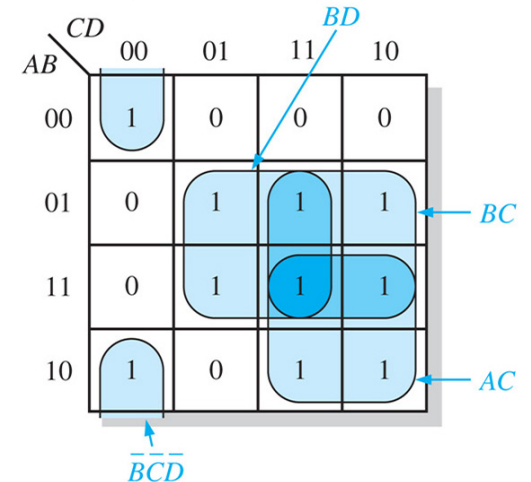

(c) Minimum SOP:  $AC + BC + BD + \bar{B}\bar{C}\bar{D}$



# The Quine-McCluskey Method (I)

- ❑ A formal tabular method for applying the Boolean distributive law to find the minimum SOP
- ❑ K-map can handle up to 4 or 5 variables but QM method can handle more
- ❑ **Step 1:** Write the function in standard minterm form and construct the truth table

**TABLE 4-9**

<i>ABCD</i>	<i>X</i>	Minterm
0000	0	
0001	1	$m_1$
0010	0	
0011	1	$m_3$
0100	1	$m_4$
0101	1	$m_5$
0110	0	
0111	0	
1000	0	
1001	0	
1010	1	$m_{10}$
1011	0	
1100	1	$m_{12}$
1101	1	$m_{13}$
1110	0	
1111	1	$m_{15}$

$$X = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + AB\bar{C}\bar{D} + ABCD$$



# The Quine-McCluskey Method (II)

- **Step 2:** Group according to the number of 1's in each minterm

**TABLE 4-10**

Number of 1s	Minterm	<i>ABCD</i>
1	$m_1$	0001
	$m_4$	0100
2	$m_3$	0011
	$m_5$	0101
	$m_{10}$	1010
	$m_{12}$	1100
3	$m_{13}$	1101
4	$m_{15}$	1111

- **Step 3:** Compare **adjacent** groups to find minterms are the same in every position except one.

**TABLE 4-11**

Number of 1s in Minterm	Minterm	<i>ABCD</i>	First Level
1	$m_1$	0001 ✓	$(m_1, m_3) 00x1$
	$m_4$	0100 ✓	$(m_1, m_5) 0x01$
2	$m_3$	0011 ✓	$(m_4, m_5) 010x$
	$m_5$	0101 ✓	$(m_4, m_{12}) x100$
	$m_{10}$	1010	$(m_5, m_{13}) x101$
	$m_{12}$	1100 ✓	$(m_{12}, m_{13}) 110x$
3	$m_{13}$	1101 ✓	$(m_{13}, m_{15}) 11x1$
4	$m_{15}$	1111 ✓	



# The Quine-McCluskey Method (III)

❑ **Step 4:** Repeat Step 5 until all groups are done

**TABLE 4-12**

First Level	Number of 1s in First Level	Second Level
$(m_1, m_3) 00x1$	1	$(m_4, m_5, m_{12}, m_{13}) x10x$
$(m_1, m_5) 0x01$		$(m_4, m_5, m_{12}, m_{13}) x10x$
$(m_4, m_5) 010x \checkmark$		
$(m_4, m_{12}) x100 \checkmark$		
$(m_5, m_{13}) x101 \checkmark$	2	
$(m_{12}, m_{13}) 110x \checkmark$		
$(m_{13}, m_{15}) 11x1$	3	

❑ **Step 5:** Write down  
the reduced expression

**TABLE 4-13**

Prime Implicants	Minterms							
	$m_1$	$m_3$	$m_4$	$m_5$	$m_{10}$	$m_{12}$	$m_{13}$	$m_{15}$
$B\bar{C} (m_4, m_5, m_{12}, m_{13})$			$\checkmark$	$\checkmark$		$\checkmark$	$\checkmark$	
$\bar{A}\bar{B}D (m_1, m_3)$	$\checkmark$	$\checkmark$						
$\bar{A}\bar{C}D (m_1, m_5)$	$\checkmark$			$\checkmark$				
$ABD (m_{13}, m_{15})$							$\checkmark$	$\checkmark$
$A\bar{B}\bar{C}\bar{D} (m_{10})$					$\checkmark$			

$$\begin{aligned}
 X &= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + AB\bar{C}\bar{D} + ABCD \\
 &= B\bar{C} + \bar{A}\bar{B}D + \bar{A}\bar{C}D + ABD + A\bar{B}\bar{C}\bar{D}
 \end{aligned}$$



# Chapter Review

## ❑ Boolean Operations and Expressions :

◆ Addition  $\rightarrow$  OR; Multiplication  $\rightarrow$  AND

## ❑ Laws and Rules of Boolean Algebra :

◆ Commutative, Associative and Distributive

◆ 12 Rules

## ❑ DeMorgan's Theorems

## ❑ Standard Forms of Boolean Expressions

◆ SOP and POS

## ❑ Boolean Expressions and Truth Tables

## ❑ The Karnaugh Map

◆ Karnaugh Map SOP Minimization

◆ Karnaugh Map POS Minimization

## ❑ The Quine-McCluskey Method

### Basic rules of Boolean algebra.

1.  $A + 0 = A$

2.  $A + 1 = 1$

3.  $A \cdot 0 = 0$

4.  $A \cdot 1 = A$

5.  $A + A = A$

6.  $A + \bar{A} = 1$

7.  $A \cdot A = A$

8.  $A \cdot \bar{A} = 0$

9.  $\bar{\bar{A}} = A$

10.  $A + AB = A$

11.  $A + \bar{A}B = A + B$

12.  $(A + B)(A + C) = A + BC$

### DeMorgan's Theorems

$$\overline{XY} = \bar{X} + \bar{Y}$$

$$\overline{X + Y} = \bar{X}\bar{Y}$$





# True/False Quiz

- ☐ Variable, complement, and literal are all terms used in Boolean algebra.
- ☐ Addition in Boolean algebra is equivalent to the NOR function.
- ☐ Multiplication in Boolean algebra is equivalent to the AND function.
- ☐ The commutative law, associative law, and distributive law are all laws in Boolean algebra.
- ☐ The complement of 0 is 0 itself.
- ☐ When a Boolean variable is multiplied by its complement, the result is the variable
- ☐ “The complement of a product of variables is equal to the sum of the complements of each variable” is a statement of DeMorgan’s theorem.
- ☐ SOP means sum-of-products.
- ☐ Karnaugh maps can be used to simplify Boolean expressions.
- ☐ A 3-variable Karnaugh map has six cells.



# True/False Quiz

- ✓ Variable, complement, and literal are all terms used in Boolean algebra.
- ✗ Addition in Boolean algebra is equivalent to the NOR function.
- ✓ Multiplication in Boolean algebra is equivalent to the AND function.
- ✓ The commutative law, associative law, and distributive law are all laws in Boolean algebra.
- ✗ The complement of 0 is 0 itself.
- ✗ When a Boolean variable is multiplied by its complement, the result is the variable
- ✓ “The complement of a product of variables is equal to the sum of the complements of each variable” is a statement of DeMorgan’s theorem.
- ✓ SOP means sum-of-products.
- ✓ Karnaugh maps can be used to simplify Boolean expressions.
- ✗ A 3-variable Karnaugh map has six cells.

